

KATHMANDU UNIVERSITY  
First internal Examination [C]  
July, 2017

JUL 11 2017

Level : B.E.  
Year : II  
Time : 2 hrs. 30 mins.

Course : EEG 202  
Semester: II  
F. M. : 55

SECTION "B"  
[5 Q. × 11 = 55 marks]

Attempt ANY FIVE questions. Figure in the margin indicates the full mark. Students are required to answer in their own words as far as practicable. Calculators are not allowed.

1.
  - a) Using  $r$ 's complement, perform the following subtraction:  
(i)  $(3250 - 72532)_{10}$  (ii)  $(72532 - 3250)_{10}$  [3]
  - b) Convert  $(3A4C.5B1)_{16}$  into decimal. [2]
  - c) Differentiate between weighted and un weighted number systems with suitable examples. [2]
  - d) Express the following Boolean function  $F = A + B'C$  in sum of minterms and product of maxterms. [4]
2.
  - a) Using K-map method, simplify the following Boolean function in (i) sum of products (ii) product of sums:  
 $F(A,B,C,D) = \sum(0,1,2,5,8,9,10)$  [5]
  - b) What is the significance of carry lookahead generator? Design a logic circuit for carry lookahead generator. [1+5]
3.
  - a) Mention some applications of decoder and draw a logic circuit for 3 to 8 line encoder. [1+3]
  - b) Write truth table and design logic circuit for 3 bit even parity generator. [5]
  - c) What are the advantages of digital system over analog system? [2]
4.
  - a) Design a logic circuit having four inputs A,B,C,D whose output is high whenever both A and B are high as long as C and D are either both low or both high. Implement the circuit using NAND gate only. [5]
  - b) Write short notes on: [3 × 2]
    - i) Johnson counter
    - ii) Master slave flip-flop
5.
  - a) Write some application of flip-flops. Derive the characteristic equation of T flip-flop and convert the JK flip-flop into D flip-flop with the help of excitation table. [1+5]
  - b) Design a logic circuit for mod-8 asynchronous up/down counters using X-OR gate and explain the operation in detail. [5]
6.
  - a) Explain the working of parallel in serial out shift register with circuit diagram. [5]
  - b) A sequential circuit has two T flip-flops A and B, one input X and output Y. The circuit is described by the following flip-flop input output equations:  
 $T_A = BX$ ,  $T_B = X$  and  $Y = AB$ . Draw the state table and state diagram of the circuit. [6]

